


PROJECT NO. – 11(b)

AIM : To construct 4X1 multiplexer


APPARATUS : input and output switch ;
NOT,AND,and OR gate


BLOCK DIAGRAM OF 4X1 MULTIPLEXER :


Block Diagram Of 4-To-1 Multiplexer

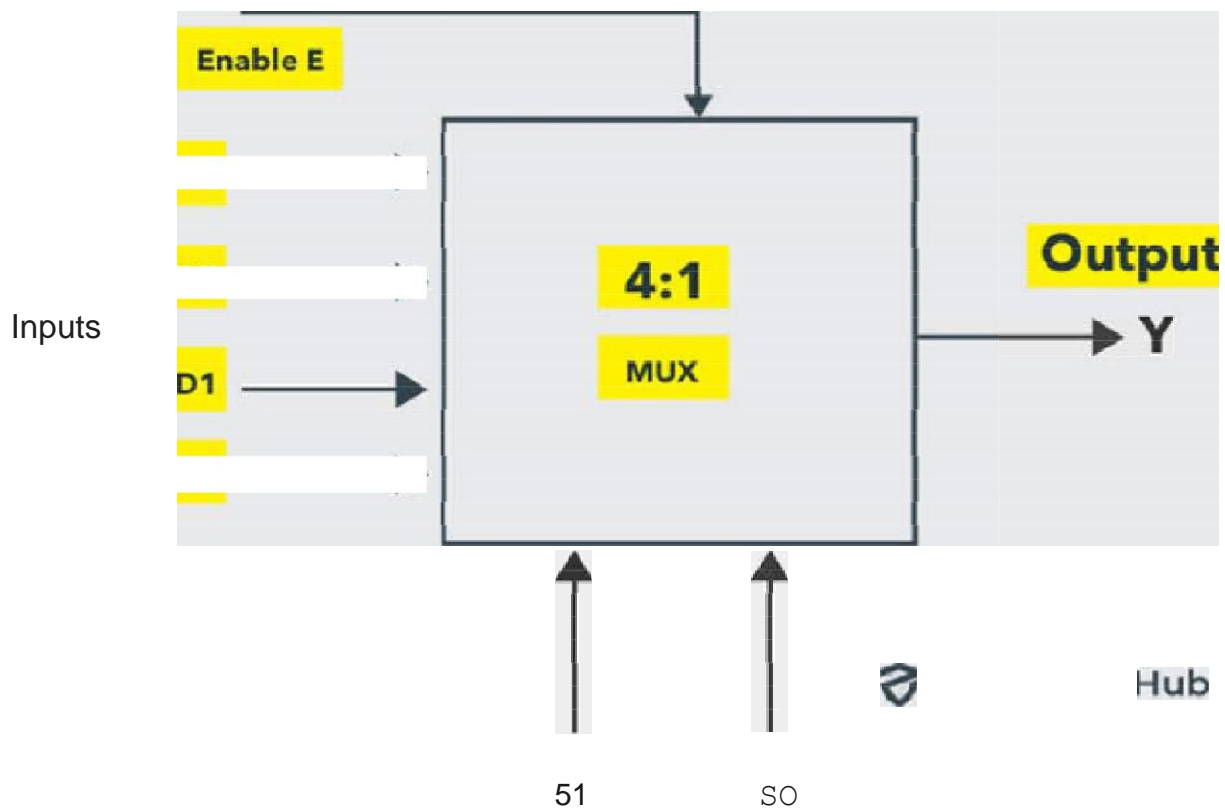


CIRCUIT DIAGRAM OF 4X1 MUX :

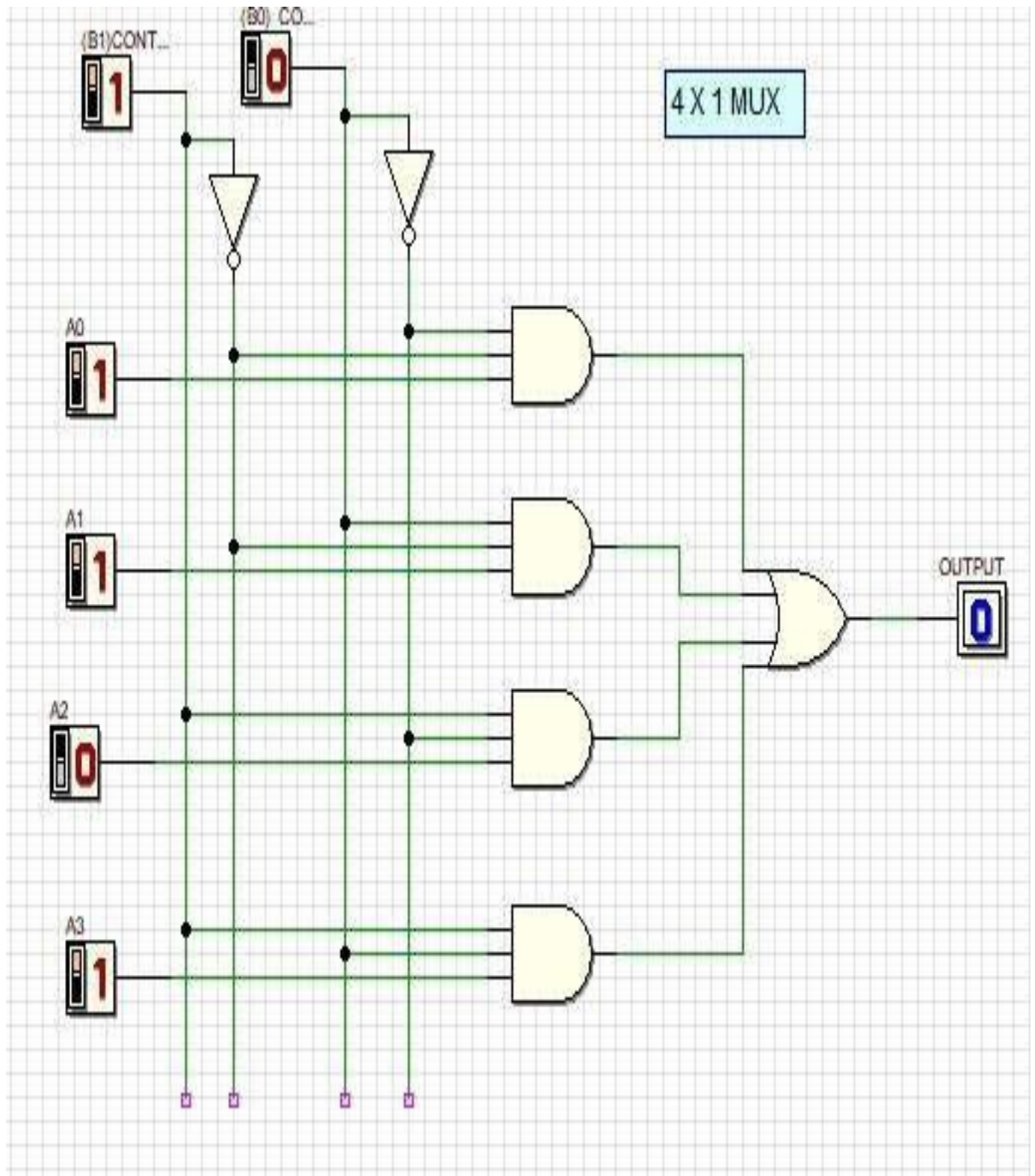

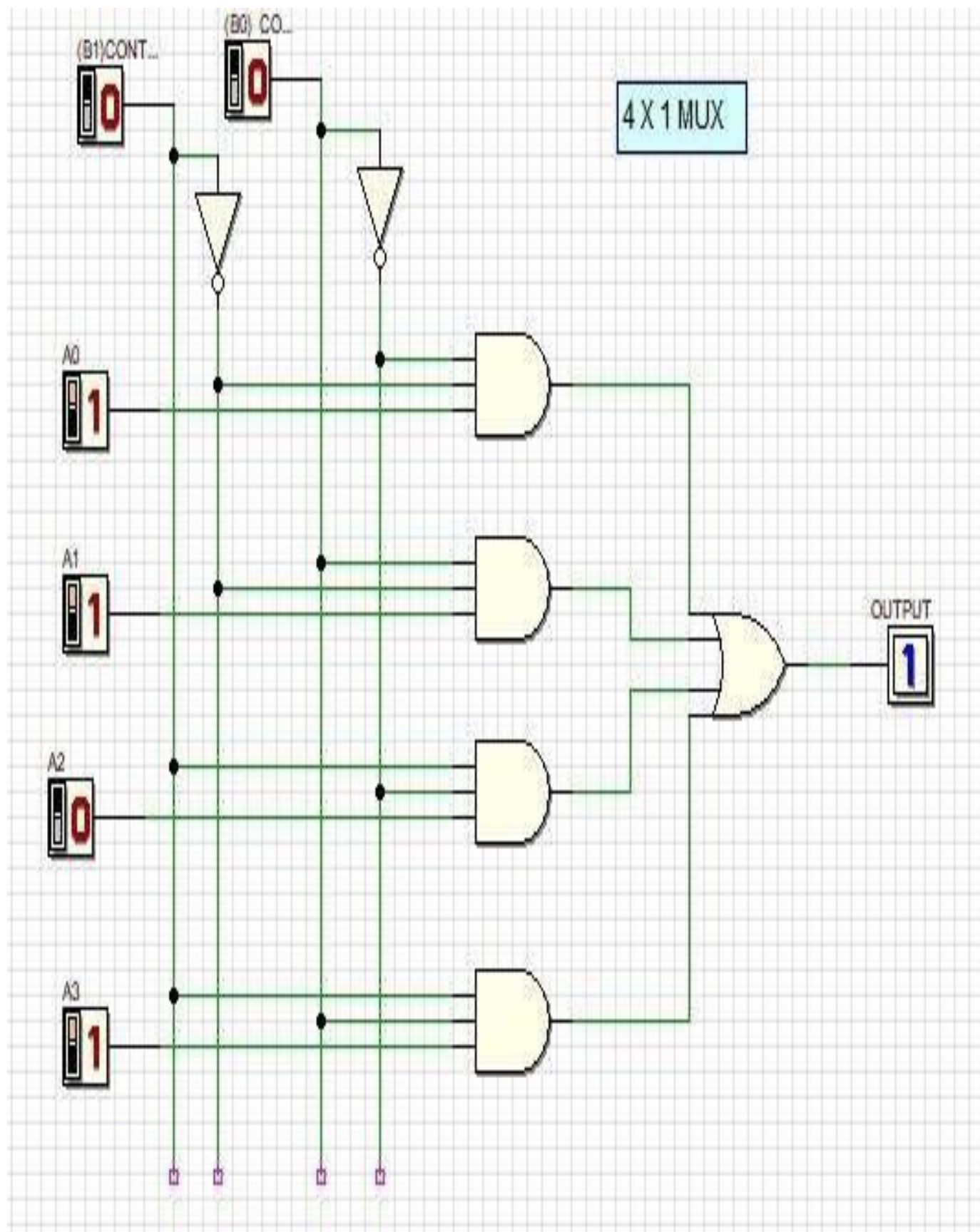

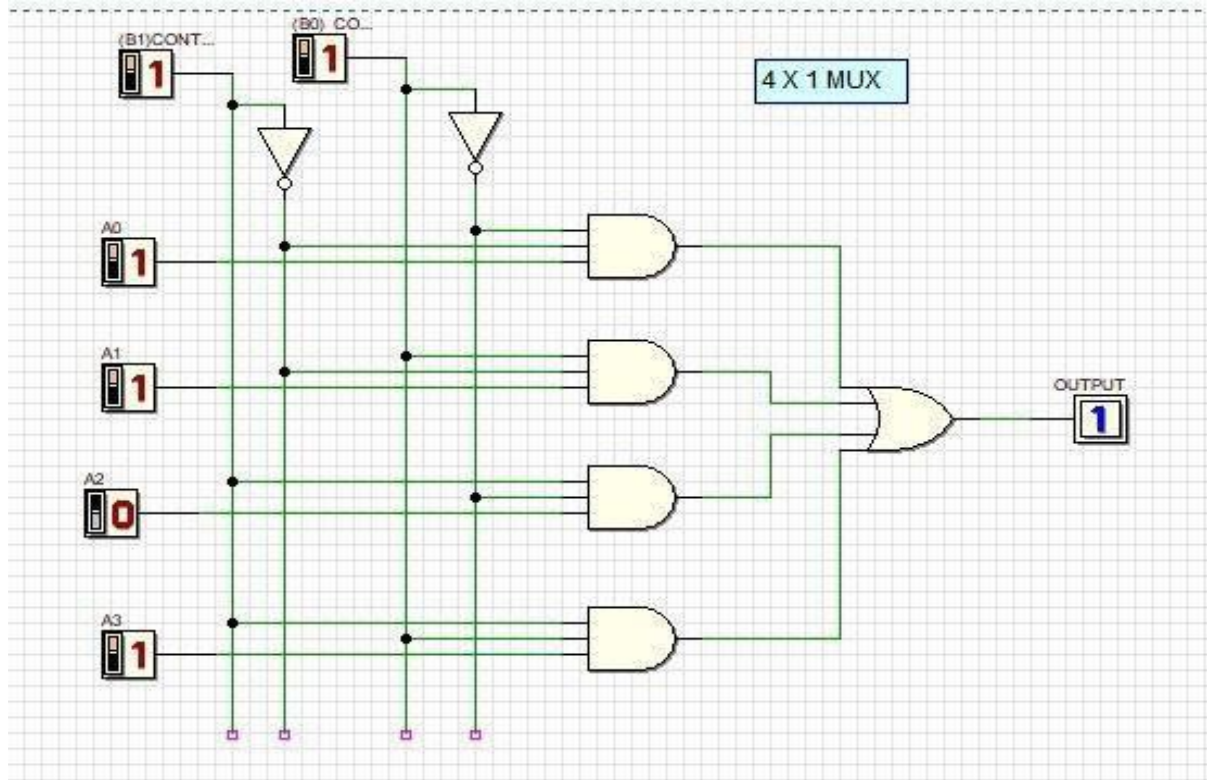

TRUTH TABLE FORN 4X1 MUX :

 

S_0	S_1	Out
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

Verilog Code:

```
//Developed by: Aashi Srivastava
// TITLE:4 to 1 mux
// Date: 15.10.23, 09.53 IST
module M4to1muxPM (
    in, sel, out
);
    input [3:0] in;
    input [1:0 ]sel;
    output reg out;

    always @(*)
    begin
        if (sel==2'b00)
            out=in[0];
        else if (sel==2'b01)
            out=in[1];
        else if (sel==2'b10)
            out=in[2];
        else
            out=in[3];
    end
endmodule
```


Test-Bench:

```
//Developed by: Aashi Srivastava
// TITLE: 4 to 1 mux test bench
// Date: 15.10.23, 09.53 IST
module M4to1muxPMTB (
);
    reg [3:0]in;
    reg [1:0]sel;
    wire out;

    M4to1muxPM M_1(in,sel,out);
    initial begin
        $dumpfile("M4to1muxPM.vcd");
        $dumpvars(0,M4to1muxPMTB);
        $monitor($time, "in=%b sel=%b out=%b", in, sel, out);
        in=4'b0011; sel=2'b00;
        #5 in=4'b0011; sel=2'b01;
        #5 in=4'b0011; sel=2'b11;
        #5 in=4'b0011; sel=2'b10;
        #20 $finish;
    end

endmodule
```

OUTPUT:

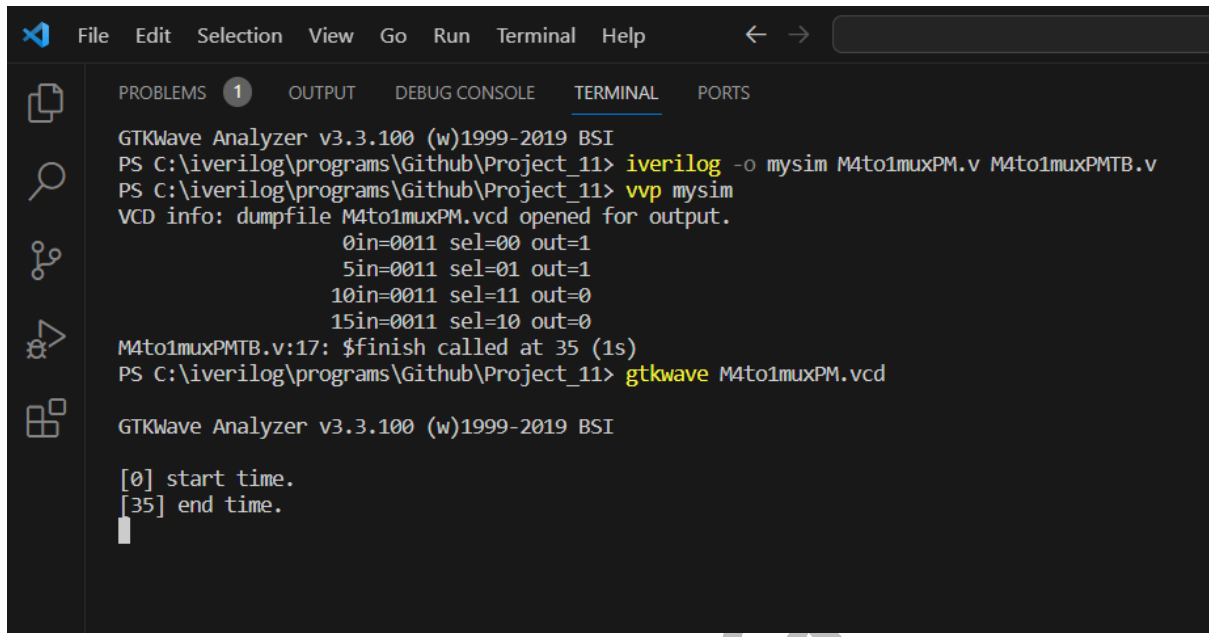

```
GTKWave Analyzer v3.3.100 (w)1999-2019 BSI
PS C:\iverilog\programs\Github\Project_11> iverilog -o mysim M4to1muxPM.v M4to1muxPMTB.v
PS C:\iverilog\programs\Github\Project_11> vvp mysim
VCD info: dumpfile M4to1muxPM.vcd opened for output.
      0in=0011 sel=00 out=1
      5in=0011 sel=01 out=1
     10in=0011 sel=11 out=0
     15in=0011 sel=10 out=0
M4to1muxPMTB.v:17: $finish called at 35 (1s)
PS C:\iverilog\programs\Github\Project_11> gtkwave M4to1muxPM.vcd

GTKWave Analyzer v3.3.100 (w)1999-2019 BSI

[0] start time.
[35] end time.
```

